



Computer Aided Design
Homework No.4

Design a generic n-bit unsigned array multiplier that multiplies 2 n-bit numbers and generates a 2n-bit output. Use FOR..GENERATE statement and test it using the Testbench.

Try to minimize the number of FOR.. GENERATE blocks.